

Diplexer design notes

Rick Karlquist, Nov. 13, 2002

Standard diplexer design is based on singly-terminated Butterworth filters. If the low pass and high pass ports are terminated in R_0 , then the input impedance of composite port will be R_0 at all frequencies. The transfer functions to the ports will be standard Butterworth responses.

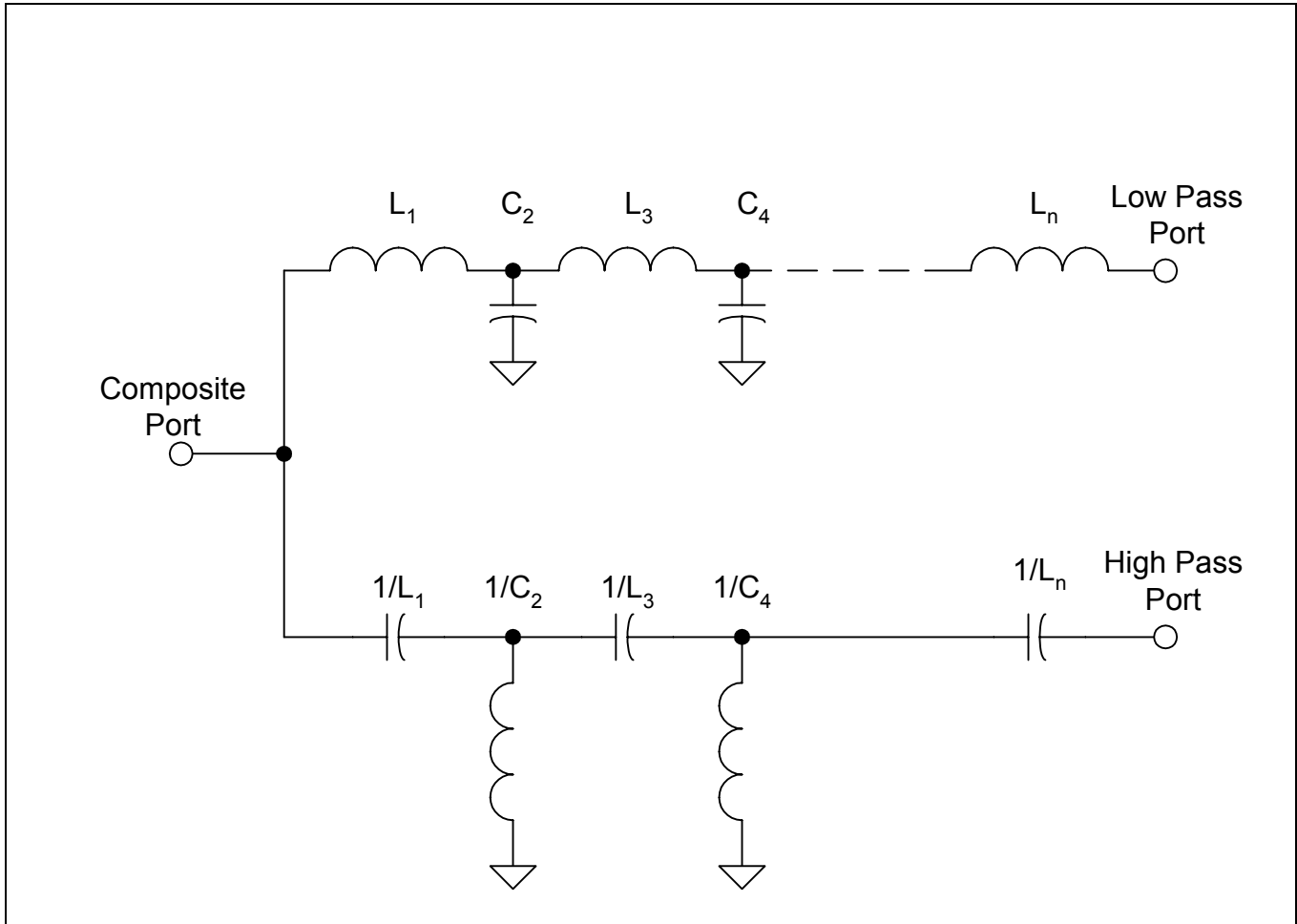


Figure 1. Prototype design for $\omega=1$, $R_0=1$.

Table 1. Singly-terminated Butterworth prototype element values.

n	L ₁	C ₂	L ₃	C ₄	L ₅	C ₆	L ₇	C ₇	L ₉	C ₁₀
1	1									
2	1.41	.707								
3	1.50	1.33	.500							
4	1.53	1.58	1.08	.383						
5	1.55	1.69	1.38	.894	.309					
6	1.55	1.76	1.55	1.20	.758	.259				
7	1.56	1.80	1.66	1.40	1.06	.656	.222			
8	1.56	1.82	1.73	1.53	1.26	.937	.578	.195		
9	1.56	1.84	1.78	1.62	1.40	1.14	.841	.516	.174	
10	1.56	1.86	1.81	1.69	1.51	1.29	1.04	.763	.465	.156

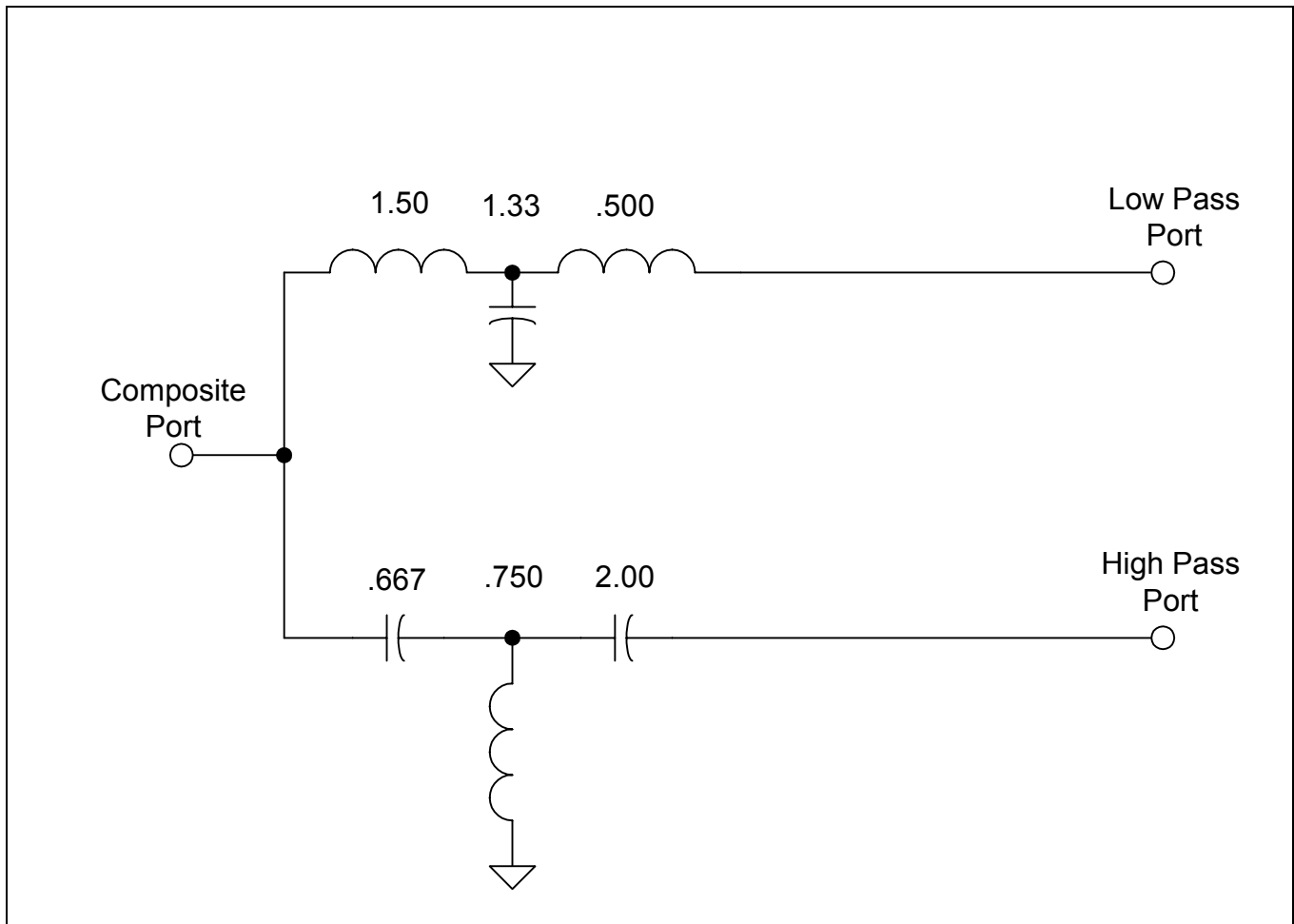


Figure 2 . Example: 3 pole prototype ($R_0 = 1, \omega=1$).

To transform prototype from $\omega=1$, $R_0 = 1$ to desired values:

Multiply prototype inductor values by: R_0/ω

Multiply prototype capacitor values by: $1/R_0\omega$

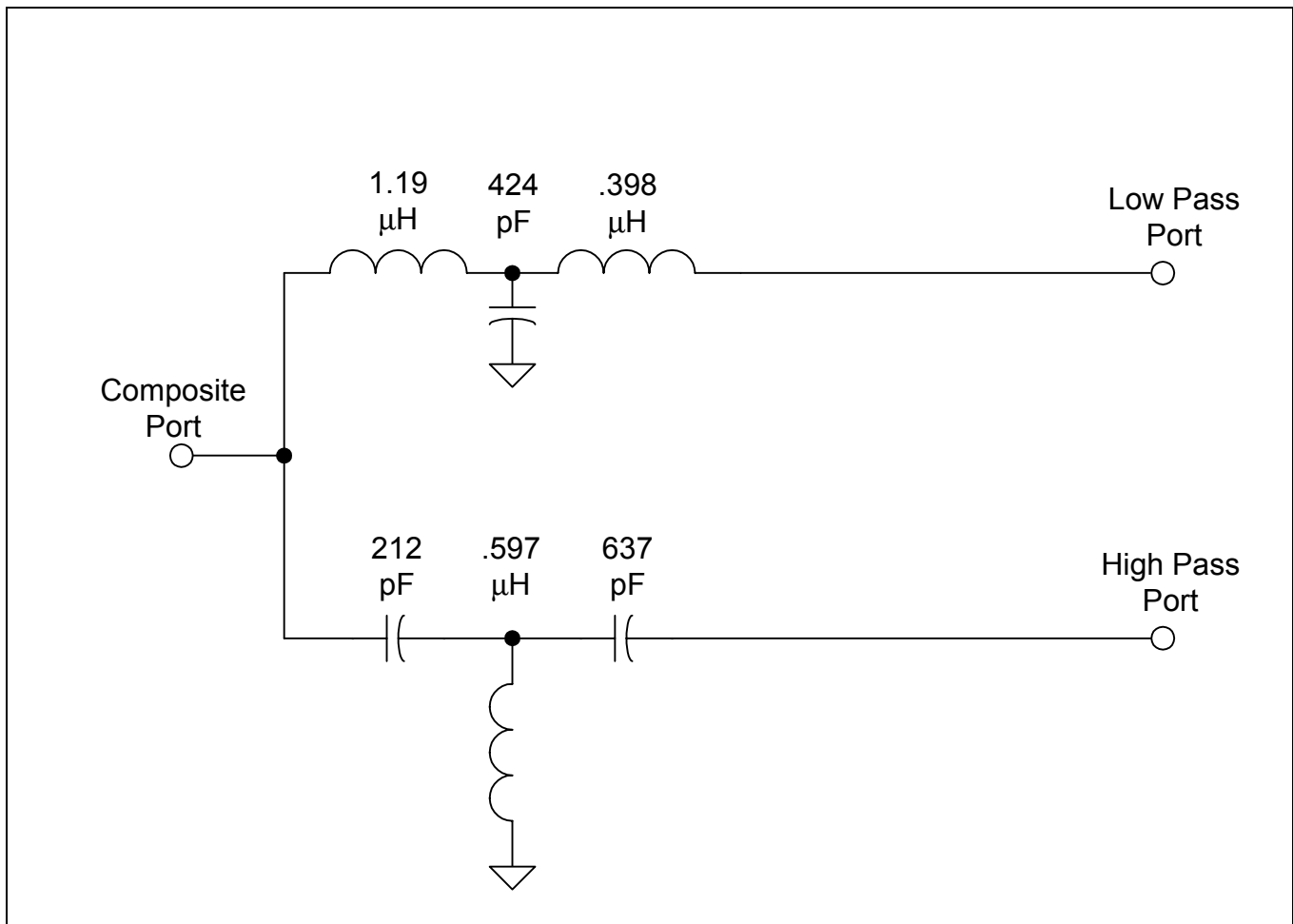


Figure 3. Example: $f = 10$ MHz and $R_0 = 50$ ohms.

[Return to N6RK home page](#)